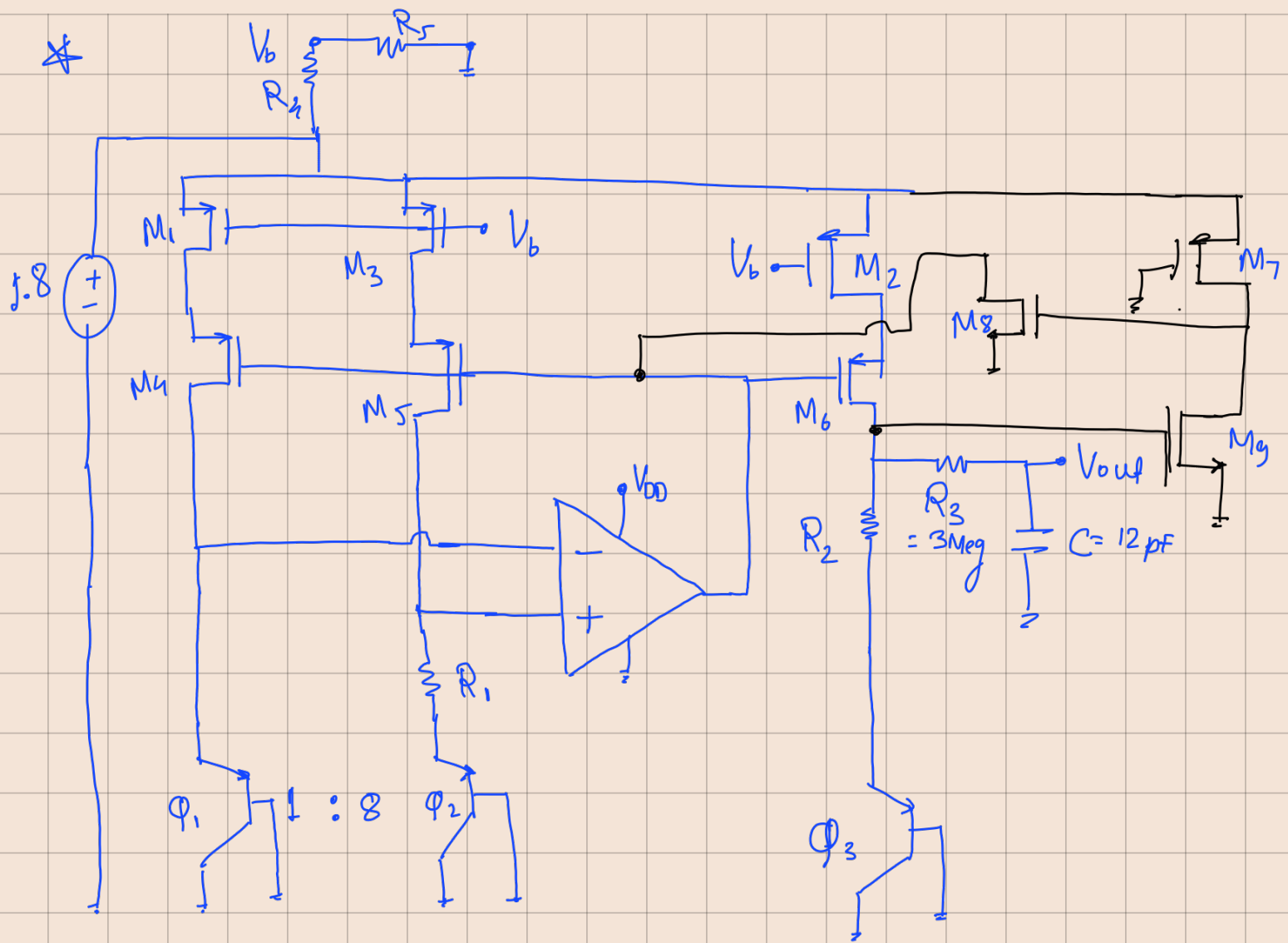
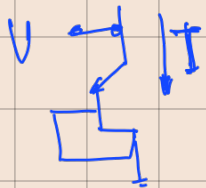




★ Calculations

- Supply voltage = 1.8V
- NMOS : $V_{TN} = 0.37\text{V}$, $\mu_n C_{ox} = 230 \mu\text{A/V}^2$
- PMOS : $V_{TP} = -0.39\text{V}$, $\mu_p C_{ox} = 100 \mu\text{A/V}^2$
- $L_{min} = 0.18 \mu\text{m}$, $W_{min} = 0.27 \mu\text{m}$
- And BJT ratio $\{n\} = 8$

→ Generating C+AT



$$\frac{\partial V_{EB}}{\partial T} \approx -2\text{mV/K}$$

→ Generating PTAT

$$\Delta V_{EB} = V_{EB2} - V_{EB1} = V_T \ln(n)$$

$$\therefore I_{PTAT} = \frac{V_T \ln(n)}{R_1}$$

→ This current is mirrored into the third branch & flows through R_2 & ρ_3

$$\therefore V_{ref} = V_{EB3} + \left(\frac{R_2}{R_1}\right) V_T \ln n$$

$$\frac{\partial V_{ref}}{\partial T} = \frac{\partial V_{EB3}}{\partial T} + \left(\frac{R_2}{R_1}\right) \ln(n) \frac{\partial V_T}{\partial T} = 0$$

$$\rightarrow \frac{\partial V_{EB}}{\partial T} = -2 \text{ mV/K}$$

$$\rightarrow \frac{\partial V_T}{\partial T} = \frac{k}{q} = 0.0862 \text{ mV/K}$$

$$\rightarrow n = 8 \Rightarrow \ln(8) = 2.079$$

$$\therefore R_2/R_1 \approx 11.17$$

⇒ Design Choice ⇒ $I_{PTAT} = 10 \mu\text{A}$

$$V_T \text{ @ } 300\text{K} \approx 26 \text{ mV}$$

$$\therefore \Delta V_{EB} = 26 \text{ mV} \cdot \ln(8) = 53.74 \text{ mV}$$

$$R_1 = \frac{\Delta V_{EB}}{I_{PTAT}} = 5.374 \text{ k}\Omega$$

$$\therefore R_2 = 11.17 \times R_1 = 60.03 \text{ k}\Omega$$

$$\text{And } V_{ref, \text{theoretical}} = V_{EB3} + I R_2 \\ = 0.65 + 10 \times 10^{-6} \times 60.03 \times 10^3$$

$$\boxed{V_{ref, \text{theoretical}} = 1.25 \text{ V}}$$

★ Biasing of transistors

→ To provide maximum voltage headroom for cascodes & the BJTs below, M_1, M_2, M_3 must act as small voltage-dropping resistors, operating deep in the linear (triode) region.

$$\rightarrow V_G = \frac{V_{DD}}{2} = 0.9V$$

→ This requires $R_4 = R_5$. To keep static power waste low, we select $R_4 = R_5 = 500k\Omega$

★ Transistor sizing

$$\begin{aligned} \rightarrow V_{SG} &= 1.8 - 0.9 = 0.9V \\ V_{SD} &= 0.1V \quad \left\{ \begin{array}{l} \text{for deep} \\ \text{triode} \end{array} \right\} \end{aligned} \quad \left\{ \begin{array}{l} V_{SD} < (V_{SG} - |V_{TP}|) \\ 0.2 < 0.51 \\ \therefore \text{linear} \end{array} \right\}$$

$$I_D \approx \mu_p C_{ox} \left(\frac{W}{L} \right) [|V_{SG} - |V_{TP}| | V_{SD}]$$

$$10 \mu A = 100 \mu A/V^2 \left(\frac{W}{L} \right) [(0.9 - 0.39) \cdot 0.1]$$

$$\Rightarrow \boxed{W/L = \frac{10}{5.1} \approx 1.96}$$

$$\therefore W = 2 \mu m \quad \& \quad L = 1 \mu m \quad \text{for} \\ M_1, M_2, M_3$$

→ for cascodes

— source node is at $1.8 - 0.1 = 1.6$

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} \times V_{ov}^2 \quad \left\{ V_{ov} = 0.2V \right\}$$

$$10 \mu A = \frac{1}{2} \times (100 \mu A/V^2) \left(\frac{W}{L} \right) (0.2V)^2$$

$$\Rightarrow \boxed{W/L = 5}$$

$\therefore W = 5 \mu m$, $L = 1 \mu m$ for
 M_4, M_5, M_6

★ Output filter

$$\begin{aligned} f_c &= \frac{1}{2\pi R_3 C_1} = \frac{1}{2 \times \pi \times 3 \times 10^6 \times 12 \times 10^{-12}} \\ &= \frac{10^6}{72 \times \pi} \approx 4.42 \text{ KHz} \end{aligned}$$

$\therefore$ High freq. noise rejected

